

# **SPICE ELECTRICAL SIMULATION**

**PHY559A**

November 18, 2024

Gabriel Pereira de Carvalho



# CONTENTS

<b>1</b>	<b>NMOS and PMOS transistors characterization</b>	<b>3</b>
1.1	$I_{DS}$ function of $V_{GS}$ . . . . .	3
1.1.1	NMOS transistor . . . . .	3
1.1.2	PMOS transistor . . . . .	4
1.2	$I_{DS}$ function of $V_{DS}$ . . . . .	5
1.2.1	NMOS transistor . . . . .	5
1.2.2	PMOS transistor . . . . .	6
<b>2</b>	<b>CMOS inverter static characterization</b>	<b>7</b>
2.1	Centered Inverter . . . . .	8
2.2	Decentered Inverter . . . . .	9
2.3	NAND2 transfer function . . . . .	11
2.3.1	Simultaneous switch . . . . .	11
2.3.2	Non-simultaneous switch . . . . .	12
<b>3</b>	<b>Dynamical characterization of the CMOS inverter</b>	<b>13</b>
3.1	Output capacitance influence . . . . .	14
3.2	W and L sizing influence . . . . .	16
3.2.1	$T_p(\text{up} \rightarrow \text{down})$ function of $W_n$ . . . . .	16
3.2.2	$T_p(\text{down} \rightarrow \text{up})$ function of $W_p$ . . . . .	18
3.3	Temperature and threshold voltage influence . . . . .	19

# 1

## NMOS AND PMOS TRANSISTORS CHARACTERIZATION

---

### 1.1 $I_{DS}$ FUNCTION OF $V_{GS}$

---

Plot, for the two types of transistors, the graph  $I_{DS}(V_{DS}, V_{GS})$  for  $V_{DS}$  constant  $= V_{DD}$ , and for  $V_{GS}$  varying between  $V_{SS}$  and  $V_{DD}$ . Define graphically the threshold voltages  $V_{tn}$  and  $V_{tp}$  of the two types of transistors.

#### 1.1.1 • NMOS TRANSISTOR

We observe that  $V_{DS} = V_{DD} \implies V_{DS} \geq V_{GS} - V_{tn} \implies$  the NMOS transistor is either cutoff or in saturation depending on the value of  $V_{GS}$ , thus

$$I_{DS}(V_{DS} = V_{DD}, V_{GS}) = \begin{cases} 0, & \text{if } V_{GS} < V_{tn} \text{ (cutoff),} \\ \frac{1}{2}k_n \frac{W}{L}(V_{GS} - V_{tn})^2, & \text{if } V_{GS} \geq V_{tn} \text{ (saturation).} \end{cases} \quad (1)$$

```

1      .include cmosws.mod
2
3      Vds 2 0 dc 3.3V
4      Vgs 1 0 dc 1V
5      M1 2 1 0 0 MODN L=0.6U W=3.0U
6
7      .dc Vgs 0 3.3 50mV
8      .end
9

```

 


Figure 1:  $I_{DS}$  function of  $V_{GS}$  for NMOS transistor

We can define  $V_{tn}$  graphically as the limit value where  $I_{DS}$  becomes greater than 0. We get

$$V_{tn} \approx 0,87$$

 


Figure 2: Determining  $V_{tn}$

### 1.1.2 • PMOS TRANSISTOR

In the PMOS transistor, to account for the reversed polarity we impose  $V_{SD} = V_{DD} \implies V_{SD} \geq V_{SG} - V_{tp}$  where  $V_{tp}$  is negative.

Now, we expect

$$I_{DS}(V_{SD} = V_{DD}, V_{SG}) = \begin{cases} 0, & \text{if } V_{SG} < |V_{tp}| \text{ (cutoff),} \\ -\frac{1}{2}k_p \frac{W}{L}(V_{SG} - |V_{tp}|)^2, & \text{if } V_{SG} \geq |V_{tp}| \text{ (saturation).} \end{cases} \quad (2)$$

```

1 .include cmosws.mod
2
3 Vsd 2 0 dc 3.3V
4 Vsg 2 1 dc 1V
5 M1 0 1 2 2 MODP L=0.6U W=6.0U
6
7 .dc Vsg 0 3.3 50mV
8 .end
9

```

Now, we can observe a curve equivalent to that of the NMOS transistor.

 


Figure 3:  $I_{DS}$  function of  $V_{SG}$  for PMOS transistor

We can identify  $|V_{tp}|$  graphically as the limit value where  $I_{DS}$  becomes smaller than 0. We get

$$V_{tp} \approx -0,82$$

## 1.2 $I_{DS}$ FUNCTION OF $V_{DS}$

Plot, for the two types of transistors, the graph  $I_{DS}(V_{DS}, V_{GS})$  for  $V_{GS}$  constant, and for  $V_{DS}$  varying between  $V_{SS}$  and  $V_{DD}$ . These plots will be done for several values of  $V_{GS}$ . Identify the linear and saturation domains for both types of transistors.

### 1.2.1 • NMOS TRANSISTOR

We will use  $V_{GS}$  equal to 1V, 2V and 3V (so we are never in the cutoff region because  $V_{GS} > V_{tn}$ ).

Theoretically we expect

$$I_{DS}(V_{DS}, V_{GS} = \text{constant}) = \begin{cases} k_n \frac{W}{L} \left[ (V_{GS} - V_{tn})V_{DS} - \frac{V_{DS}^2}{2} \right], & \text{if } V_{DS} < V_{GS} - V_{tn} \text{ (triode or linear),} \\ \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_{tn})^2, & \text{if } V_{GS} \geq V_{tn} \text{ (saturation).} \end{cases} \quad (3)$$

```

1 .include cmosws.mod
2
3 Vds 2 0 dc 3.3V

```

```

4 Vgs 1 0 dc 1V
5 M1 2 1 0 0 MODN L=0.6U W=3.0U
6
7 .dc Vds 0 3.3 50mV Vgs 1 3 1V
8 .end
9

```

 


Figure 4:  $I_{DS}$  function of  $V_{DS}$  for NMOS transistor

### 1.2.2 • PMOS TRANSISTOR

Once again for the PMOS, we make adaptations to account for reversed polarity.

We will use  $V_{SG}$  equal to 1V, 2V and 3V (so we are never in the cutoff region because  $V_{SG} > |V_{tp}|$ ).

Theoretically we expect

$$I_{DS}(V_{SD}, V_{SG} = \text{constant}) = \begin{cases} -k_p \frac{W}{L} \left[ (V_{SG} - |V_{tp}|) V_{SD} - \frac{V_{SD}^2}{2} \right], & \text{if } V_{SD} < V_{SG} - |V_{tp}| \text{ (triode or linear),} \\ -\frac{1}{2} k_p \frac{W}{L} (V_{SG} - |V_{tp}|)^2, & \text{if } V_{SG} \geq |V_{tp}| \text{ (saturation).} \end{cases} \quad (4)$$

```

1 .include cmosws.mod
2
3 Vsd 2 0 dc 3.3V
4 Vsg 2 1 dc 1V
5 M1 0 1 2 2 MODP L=0.6U W=6.0U
6
7 .dc Vsd 0 3.3 50mV Vsg 1 3 1V
8 .end
9

```


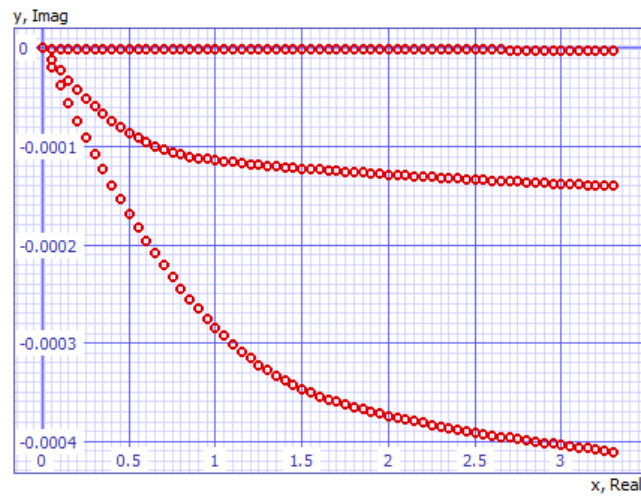


Figure 5:  $I_{DS}$  function of  $V_{SD}$  for PMOS transistor

## 2

# CMOS INVERTER STATIC CHARACTERIZATION

 

## 2.1 CENTERED INVERTER

Plot the static transfer function for a centered inverter. Deduce the noise margin on the input low state and high state.

```

1      .include cmosws.mod
2
3      Vin 1 0 dc 1V
4      Vdd 2 0 dc 3.3V
5      M1 3 1 0 0 MODN L=0.6U W=3.0U
6      M2 2 1 3 2 MODP L=0.6U W=6.0U
7
8      .dc Vin 0 3.3 50mV
9      .end
10

```



Figure 6: Transfer function for centered inverter

From the graphic, we have

- $V_{IL} = 0,92V$  (maximum  $V_{in}$  for which  $V_{out}$  is high)
- $V_{IH} = 2,3V$  (minimum  $V_{in}$  for which  $V_{out}$  is low)
- and we consider  $V_{OL} = 0V$  and  $V_{OH} = 3,3V$ .

We conclude that

- $NML = V_{IL} - V_{OL} = 0,92V$
- $NMH = V_{OH} - V_{IH} = 3,3 - 2,3 = 1V$

We observe that  $W_p = 2W_n$  did not give us a perfectly centered inverter, we expected  $NML = NMH$ .



## 2.2 DECENTERED INVERTER

Plot the transfer function for a decentered inverter with

- $W_n = W_p = 3,0\mu m$
- $W_p = 12,0\mu m$  and  $W_n = 3,0\mu m$

Deduce the noise margins on the input low state and high state.

For a lower value of  $W_p$ , the PMOS transistor has a smaller  $g_m = \frac{\partial I_D}{\partial V_{SG}} = k_p \frac{W}{L} (V_{SG} - |V_{tp}|)$ . Thus, the PMOS is less sensitive to variations in  $V_{SG}$  which makes the high-low transition slower. We expect  $NML < NMH$ .



Figure 7: Transfer function for decentered inverter with  $W_n = W_p = 3,0\mu m$

We get from the graphic

- $V_{IL} = 0,85V$  (maximum  $V_{in}$  for which  $V_{out}$  is high)
- $V_{IH} = 2,22V$  (minimum  $V_{in}$  for which  $V_{out}$  is low)
- again we consider  $V_{OL} = 0V$  and  $V_{OH} = 3,3V$ .

We conclude that

- $NML = V_{IL} - V_{OL} = 0,85V$
- $NMH = V_{OH} - V_{IH} = 3,3 - 2,22 = 1,08V$

Now for a higher value of  $W_p$ , the PMOS transistor has a higher  $g_m = \frac{\partial I_D}{\partial V_{SG}} = k_p \frac{W}{L} (V_{SG} - |V_{tp}|)$ . Thus, the PMOS is more sensitive to variations in  $V_{SG}$  which makes the high-low transition faster. We expect  $NML > NMH$ .



Figure 8: Transfer function for decentered inverter with  $W_p = 12,0\mu m$  and  $W_n = 3,0\mu m$


We get from the graphic

- $V_{IL} = 0,99V$  (maximum  $V_{in}$  for which  $V_{out}$  is high)
- $V_{IH} = 2,35V$  (minimum  $V_{in}$  for which  $V_{out}$  is low)
- again we consider  $V_{OL} = 0V$  and  $V_{OH} = 3,3V$ .

We conclude that

- $NML = V_{IL} - V_{OL} = 0,99V$
- $NMH = V_{OH} - V_{IH} = 3,3 - 2,35 = 0,95V$

## 2.3 NAND2 TRANSFER FUNCTION

 

Plot the static transfer function of the NAND2 gate in the following cases:

- The entries  $A$  and  $B$  of this NAND gate are connected to the same input signal which varies from  $V_{SS}$  to  $V_{DD}$ . In this scenario the two inputs switch at the same time.
- The  $A$  input is at high state (voltage  $V_{DD}$ ), and the  $B$  voltage varies from  $V_{SS}$  to  $V_{DD}$ . This corresponds to commutations which do not occur at the same time.

Deduce the noise margin on the input low state and high state.

### 2.3.1 • SIMULTANEOUS SWITCH

We observe that  $A = B = 0 \implies A \cdot B = 1$  and  $A = B = 1 \implies A \cdot B = 0$ . Thus, we expect the output graphic to look like an inverter and we can compute the margins like we did in the previous question.

```

1      .include cmosws.mod
2
3      Vdd 1 0 dc 3.3V
4      Vin 2 0 dc 1.0V
5      M1 1 2 4 1 MODP L=0.6U W=6.0U
6      M2 1 2 4 1 MODP L=0.6U W=6.0U
7      M3 4 2 5 0 MODN L=0.6U W=6.0U
8      M4 5 2 0 0 MODN L=0.6U W=6.0U
9
10     .dc Vin 0 3.3 50mV
  
```

```
.end
```

 


Figure 9: In red, we have inputs A and B. In green the output of the NAND2 gate.

We get from the graphic

- $V_{IL} = 0,97V$  (maximum  $A, B$  for which  $V_{out}$  is high)
- $V_{IH} = 2,32V$  (minimum  $A, B$  for which  $V_{out}$  is low)
- again we consider  $V_{OL} = 0V$  and  $V_{OH} = 3,3V$ .

We conclude that

- $NML = V_{IL} - V_{OL} = 0,97V$
- $NMH = V_{OH} - V_{IH} = 3,3 - 2,32 = 0,98V$

### 2.3.2 • NON-SIMULTANEOUS SWITCH

Now we fix  $A = 1$ . For  $B = 0$ , we have  $A \cdot B = 1$  and for  $B = 1$ , we have  $A \cdot B = 0$ . Thus, if we consider  $V_{in} = B$  we have once again an inverter and we can compute the margins like we did previously.

```
.include cmosws.mod
Vdd 1 0 dc 3.3V
Va 2 0 dc 3.3V
Vb 3 0 dc 1.0V
M1 1 2 4 1 MODP L=0.6U W=6.0U
M2 1 3 4 1 MODP L=0.6U W=6.0U
M3 4 2 5 0 MODN L=0.6U W=6.0U
```

```

9      M4  5 3 0 0 MODN L=0.6U W=6.0U
10
11      .dc Vb 0 3.3 50mV
12      .end
13

```

 


Figure 10: In red, we have input B. In green the output of the NAND2 gate.

We get from the graphic

- $V_{IL} = 0,87V$  (maximum  $A, B$  for which  $V_{out}$  is high)
- $V_{IH} = 2,31V$  (minimum  $A, B$  for which  $V_{out}$  is low)
- again we consider  $V_{OL} = 0V$  and  $V_{OH} = 3,3V$ .

We conclude that

- $NML = V_{IL} - V_{OL} = 0,87V$
- $NMH = V_{OH} - V_{IH} = 3,3 - 2,31 = 0,99V$

Comparing the margins calculated, we conclude that the simultaneous switch gives a more centered curve.

### 3

## DYNAMICAL CHARACTERIZATION OF THE CMOS INVERTER

## 3.1 OUTPUT CAPACITANCE INFLUENCE

We consider a centered CMOS inverter for which the output  $S$  is connected to a charge capacitance  $C$ . This capacitance  $C$  modeled the sum of the capacitance of the input gates addressed by the signal  $S$ , plus the interconnection capacitance. We now use

- $L_n = 0,6\mu m$  and  $W_n = 3,0\mu m$ ;
- $L_p = 0,6\mu m$  and  $W_p = 6,0\mu m$ ;


Measure the propagation time  $T_p(\text{up} \rightarrow \text{down})$  and  $T_p(\text{down} \rightarrow \text{up})$  for  $C$  equal to  $0.0pF$ ,  $0.1pF$ ,  $0.2pF$ ,  $0.5pF$  and  $1.0pF$ .  
Plot  $T_p(C)$ .

We modify the code for the centered inverter to introduce the capacitance  $C$ . I could not find support for *parameter sweep* in Spice Opus, so we must run the script with a different value of  $C$  to measure each propagation time.

```

1      .include cmosws.mod
2
3      Vin 1 0 pulse(0.0V 3.3V 5ns 1ns 1ns 3ns 8ns)
4      Vdd 2 0 dc 3.3V
5      M1 3 1 0 0 MODN L=0.6U W=3.0U
6      M2 2 1 3 2 MODP L=0.6U W=6.0U
7      C1 3 0 0.0pF
8      *C1 3 0 0.1pF
9      *C1 3 0 0.2pF
10     *C1 3 0 0.5pF
11     *C1 3 0 1.0pF
12
13     .tran 0.05ns 13ns
14     .end
15

```

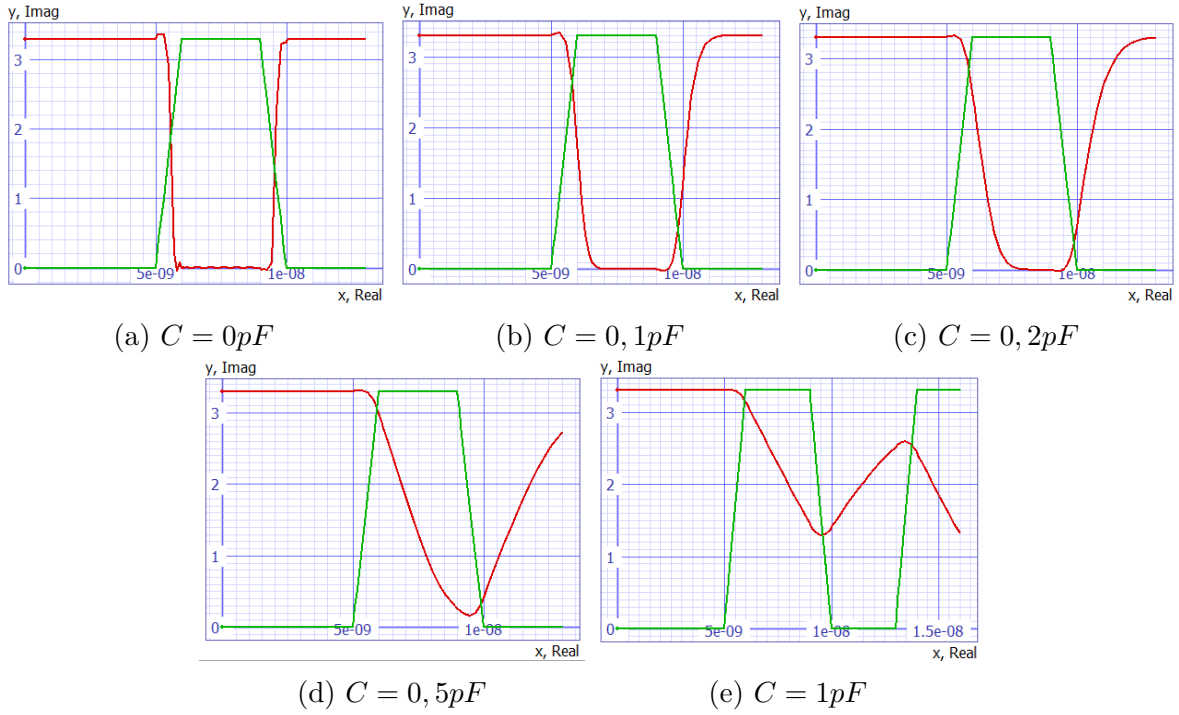Figure 11: Output  $V_{out}$  in red and input  $V_{in}$  in green for different values of  $C$ 

$C$	$T_p(\text{up} \rightarrow \text{down})$	$T_p(\text{down} \rightarrow \text{up})$
$0pF$	0, 11ns	0, 12ns
$0, 1pF$	0, 52ns	0, 62ns
$0, 2pF$	0, 81ns	1, 02ns
$0, 5pF$	1, 69ns	1, 82ns
$1pF$	3, 11ns	1, 08ns

Table 1: Propagation times measured in each plot

When we plot the propagation times, we observe a clear linear relation between  $T_p$  and  $C$ . We can use linear regression to plot  $T_p(\text{up} \rightarrow \text{down})$  and  $T_p(\text{down} \rightarrow \text{up})$ . For high values of  $C$  however, it is importance to notice that because the capacitor never manages to fully discharge,  $T_p(\text{down} \rightarrow \text{up})$  starts to decrease and we lose this linear behavior. The plot was made using *Python*.

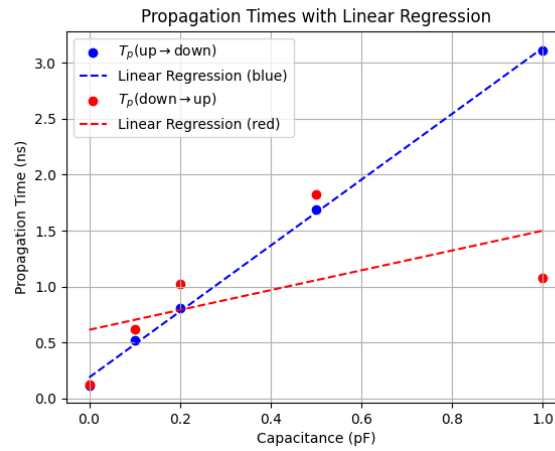


Figure 12: Propagation time  $T_p$  as function of capacitance  $C$

## 3.2 W AND L SIZING INFLUENCE

We select a charge capacitance of  $0,5pF$ .

- Measure the variation of the propagation times when the resistance of the N transistor is decreased by increasing  $W_n$ . Plot the graph  $T_p^{\text{up} \rightarrow \text{down}}(W_n)$ .
- Measure the variation of the propagation times when the resistance of the N transistor is decreased by increasing  $W_n$ . Plot the graph  $T_p^{\text{down} \rightarrow \text{up}}(W_p)$ .

### 3.2.1 • $T_p(\text{UP} \rightarrow \text{DOWN})$ FUNCTION OF $W_n$

The values of  $W_n$  chosen for simulation and measurement were:  $2\mu m$ ,  $3\mu m$ ,  $6\mu m$ ,  $9\mu m$ ,  $12\mu m$ . I tried  $W_n = 1\mu m$  but for low values of  $W_n$ , the output does not even reach  $\frac{V_{DD}}{2}$ .

$W_n$	$T_p(\text{up} \rightarrow \text{down})$
$2\mu m$	$2,48ns$
$3\mu m$	$1,69ns$
$6\mu m$	$0,91ns$
$9\mu m$	$0,69ns$
$12\mu m$	$0,56ns$

Table 2: Propagation time measured for each value of  $W_n$



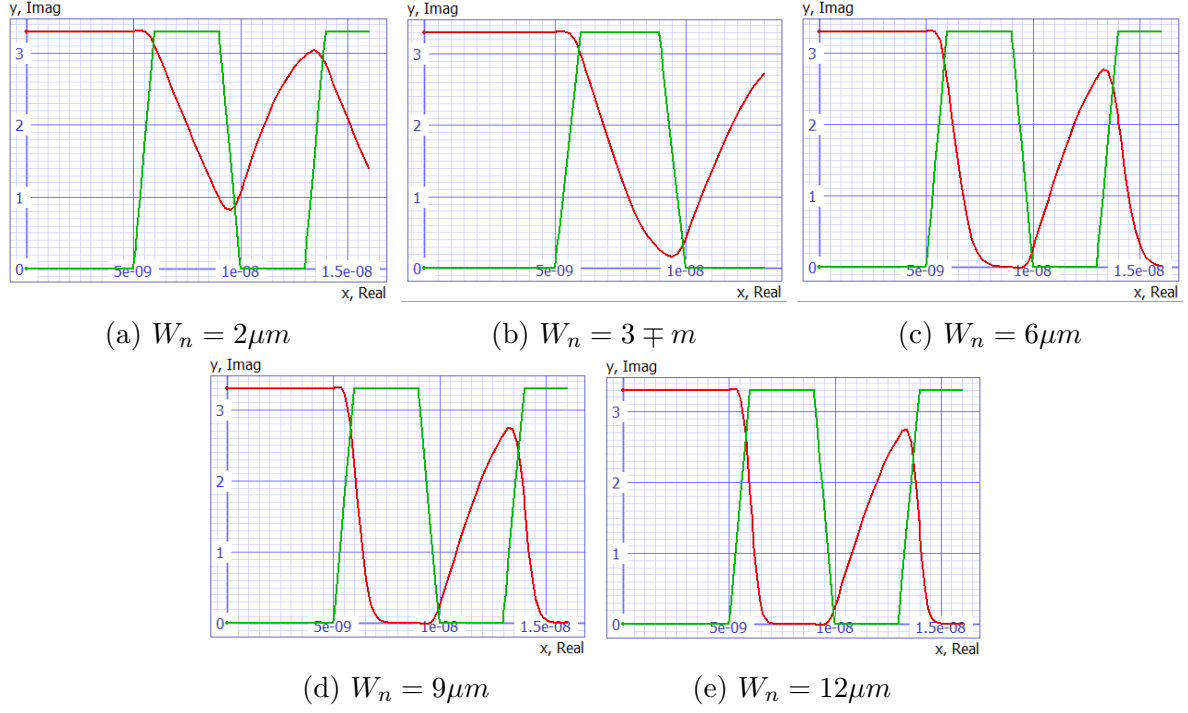


Figure 13: Output  $V_{out}$  in red and input  $V_{in}$  in green for different values of  $W_n$

When we plot  $T_p(\text{up} \rightarrow \text{down})$  as a function of  $W_n$ , we observe that  $T_p(\text{up} \rightarrow \text{down})$  seems to decrease exponentially and for large values of  $W_n$  it approaches some constant. Therefore, the appropriate fit is

$$T_p^{\text{up} \rightarrow \text{down}}(W_n) = a \cdot e^{-bW_n} + c$$

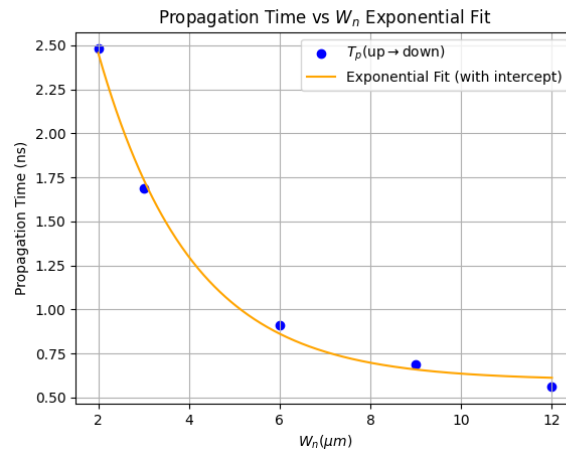


Figure 14: Propagation time  $T_p(\text{up} \rightarrow \text{down})$  as function of  $W_n$

### 3.2.2 • $T_p(\text{DOWN} \rightarrow \text{UP})$ FUNCTION OF $W_p$

The values of  $W_p$  chosen for simulation and measurement were:  $4\mu m$ ,  $5\mu m$ ,  $6\mu m$ ,  $9\mu m$ ,  $12\mu m$ . I tried  $W_p = 3\mu m$  but similarly to what we verified for  $W_n$ , for low values of  $W_p$ , the output does not even reach  $\frac{V_{DD}}{2}$ .

$W_p$	$T_p(\text{down} \rightarrow \text{up})$
$4\mu m$	$2,82ns$
$5\mu m$	$2,22$
$6\mu m$	$1,81ns$
$9\mu m$	$1,31ns$
$12\mu m$	$1,01ns$

Table 3: Propagation time measured for each value of  $W_p$

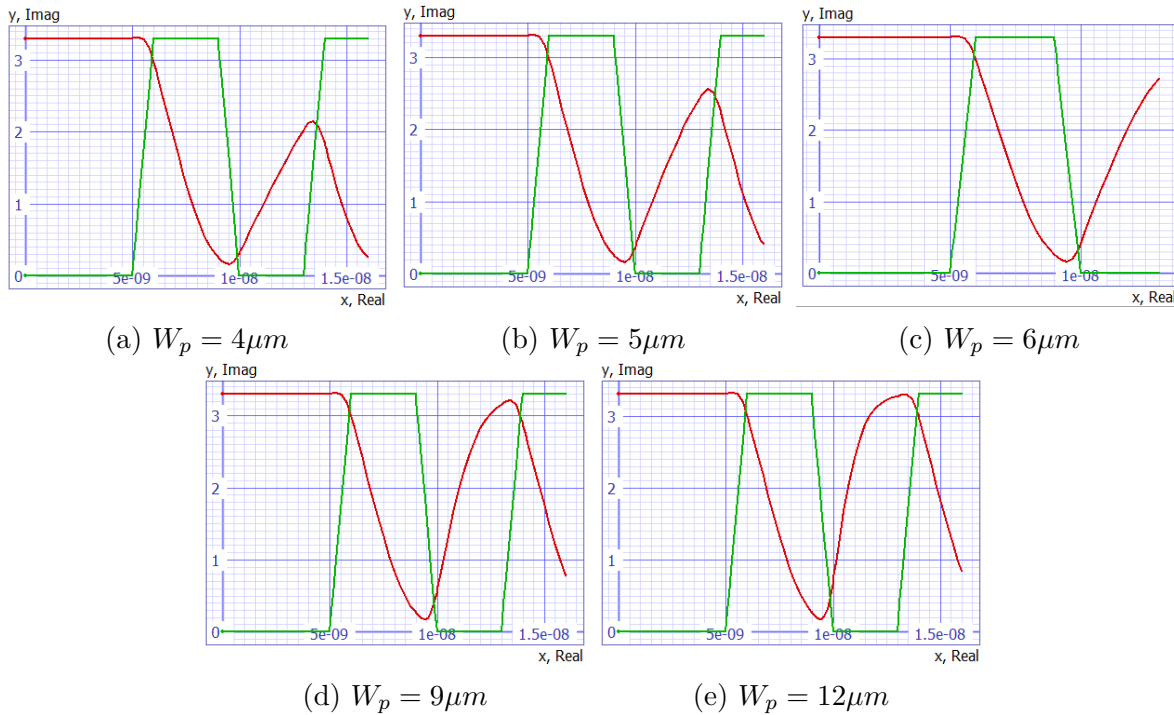


Figure 15: Output  $V_{out}$  in red and input  $V_{in}$  in green for different values of  $W_p$

Now, when we plot  $T_p(\text{down} \rightarrow \text{up})$  as a function of  $W_p$ , we observe that  $T_p(\text{down} \rightarrow \text{up})$  seems to decrease exponentially and for large values of  $W_p$  it approaches some constant. Therefore, the appropriate fit is

$$T_p^{\text{down} \rightarrow \text{up}}(W_p) = a \cdot e^{-bW_p} + c$$

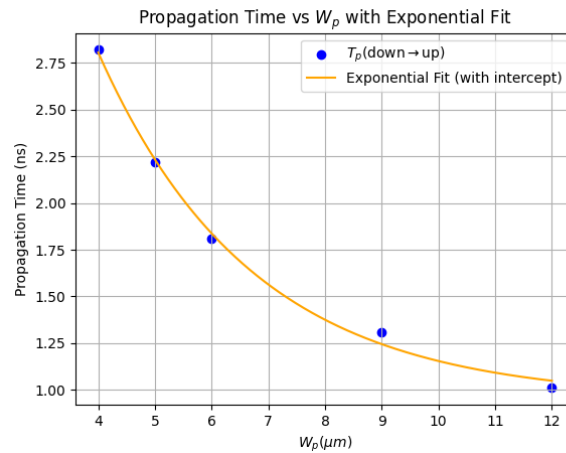


Figure 16: Propagation time  $T_p(\text{down} \rightarrow \text{up})$  as function of  $W_p$

### 3.3 TEMPERATURE AND THRESHOLD VOLTAGE INFLUENCE

Measure the variation of the propagation time for the reference inverter ( $W_n = 3\mu m$  and  $W_p = 6\mu m$ ) for an output capacitance  $C$  of  $0,5pF$  in the four following cases:

- $-40^\circ C$ , worst case
- $+125^\circ C$ , worst case
- $-40^\circ C$ , typical
- $+125^\circ C$ , typical

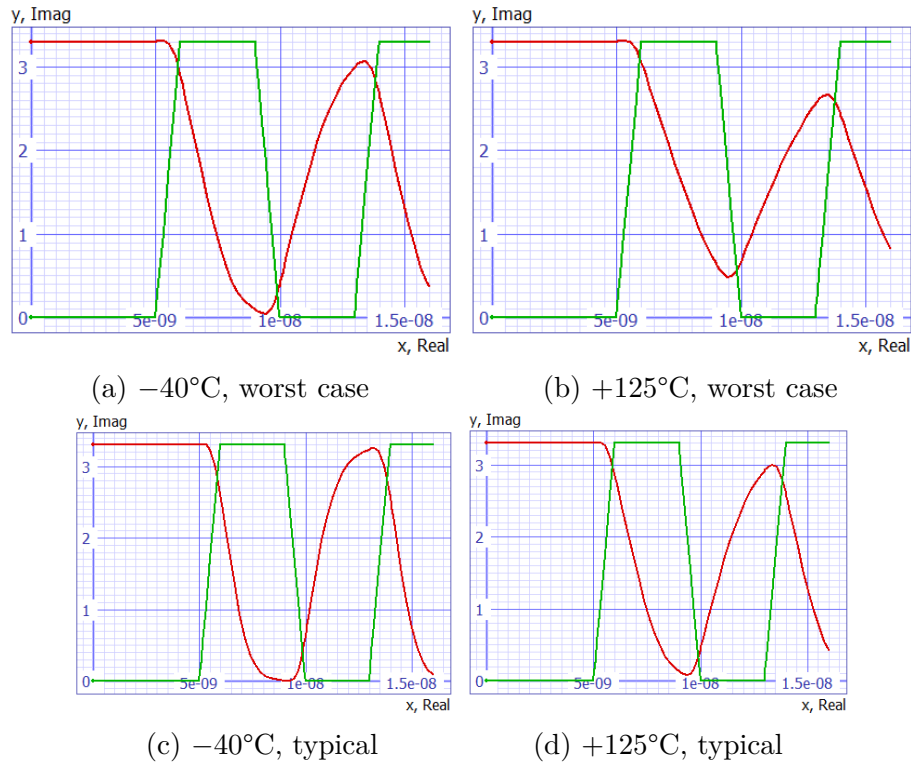


Figure 17: Output  $V_{out}$  in red and input  $V_{in}$  in green in all 4 scenarios

	$-40^{\circ}\text{C}$	$+125^{\circ}\text{C}$
worst case	1,43ns	2,07ns
typical	0,99ns	1,43ns

Table 4:  $T_p(\text{down} \rightarrow \text{up})$  measured in all 4 scenarios

	$-40^{\circ}\text{C}$	$+125^{\circ}\text{C}$
worst case	1,61ns	1,91ns
typical	1,11ns	1,61ns

Table 5:  $T_p(\text{up} \rightarrow \text{down})$  measured in all 4 scenarios

We observe that  $T_p(\text{down} \rightarrow \text{up})$  and  $T_p(\text{up} \rightarrow \text{down})$  are bigger for the worst case parameters as expected. And they are also bigger at higher temperatures, which we also expected because heating causes the transistor's performance to deteriorate.